

Checklist: Lab 6

PHOTOGRAPH AND UPLOAD TO ELMS AT END OF EACH WORKING SESSION

Your in-class grade is based mainly on this checklist. After completing each part, be sure to get your instructor to sign off. If the work is not correct, your instructor will discuss your work with you and give you hints to correct it. You can then correct your work and ask again for sign off. You can do this as many times as necessary, until the work is correct. There is no penalty for number of attempts.

■ SL1, SL1.1 transistor array

- predicted the differential and common-mode gains and
- wire SL1

■ special instructions in supplement labeled “setup the input circuit, and check the transformer” and SL1.4

- Setup circuit in fig SL1.7 except not yet attaching the transformer to the differential amplifier inputs A and B
- Show via photos that the output of the transformer is behaving as expected.
- Measure the common mode and differential gain of just the transformer.

■ SL1.5 differential amplifier with 10kohm resistor

- Common-mode gain
- Differential gain

■ SL1.5 with JFET

- Common-mode gain
- Differential gain