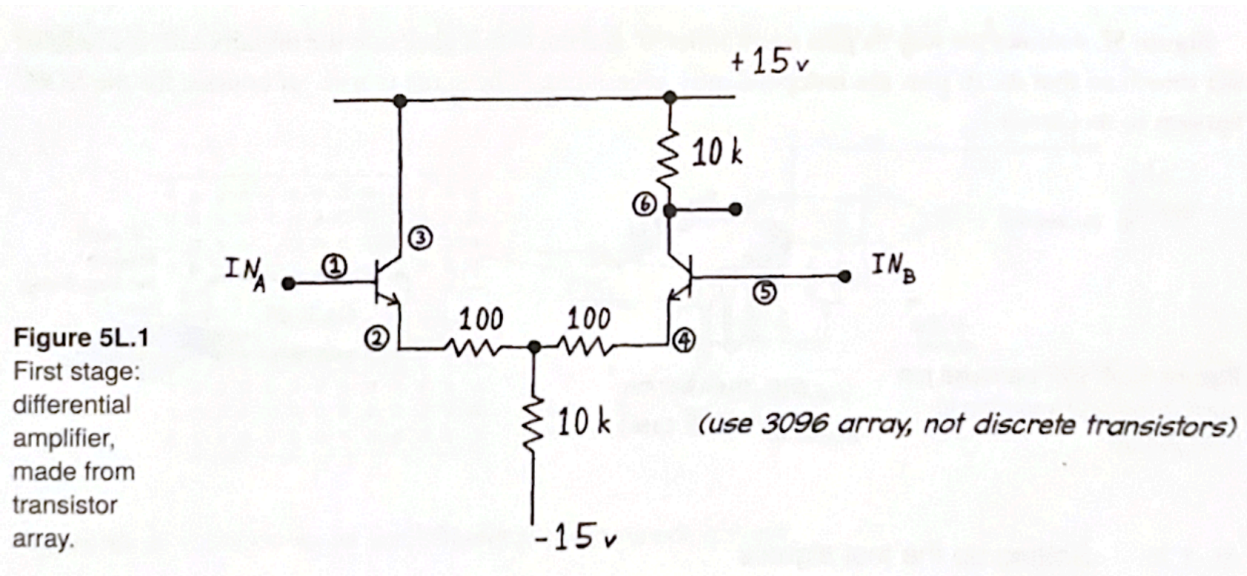



☐ 5L.1, 5L1.1 transistor array

- ☐ Predicted the differential and common-mode gains and measured
- ☐ wire 5L.1



☐ Special instructions in supplement labeled “set up the input circuit, and check the transformer” and 5L.1.4

- ☐ Set up the circuit in fig 5L.7, except not yet attaching the transformer to the differential amplifier inputs A and B

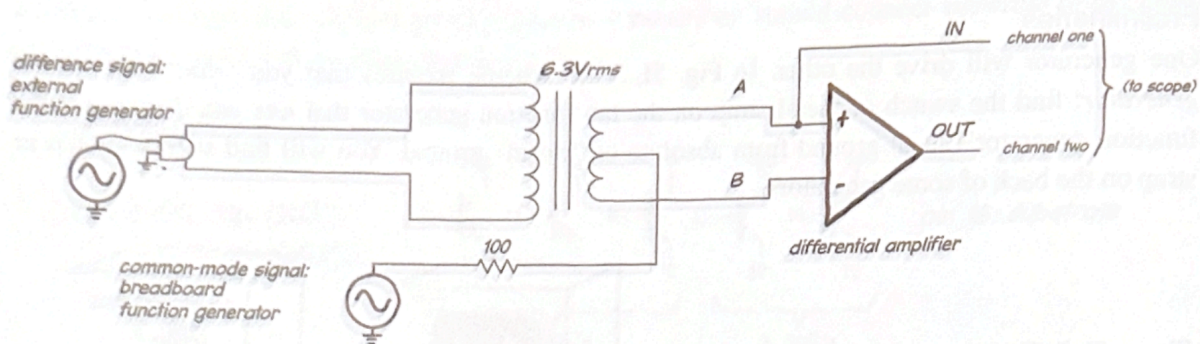

**Figure 5L.7** Transformer allows two function generators to provide separate *differential* and *common-mode* signal sources.

- ☐ Show via photos that the output of the transformer is behaving as expected.
- ☐ Measure the common-mode and differential gain of just the transformer.

☐ 5L.1.5 differential amplifier with 10kohm resistor

- ☐ Common-mode gain
- ☐ Differential gain

☐ 5L.1.5 with JFET

- ☐ Common-mode gain
- ☐ Differential gain