

Date
09/09/2026

Your section number

Your name
Darius Gichuru

Checklist: Lab 2

PHOTOGRAPH AND UPLOAD TO ELMS AT END OF EACH WORKING SESSION

Your in-class grade is based mainly on this checklist. After completing each part, be sure to get your instructor to sign off. If the work is not correct, your instructor will discuss your work with you and give you hints to correct it. You can then correct your work and ask again for sign off. You can do this as many times as necessary, until the work is correct. There is no penalty for number of attempts.

☒ 1L.5 diode

- Two plots (lin, log)

☒ 1L.6 I-V curve mystery box

- Questions: if volt too high, voltage on front face, ohm's law
- Dynamic resistance

☒ 1L.7 scope and function generator

- Sine wave
- Output impedance of function generator

☒ 2L.1.1 RC circuit time constant

- Waveform
- RC time constant

☐ wheatstone bridge

- Thermistor resistance with ohm meter
- How close to zero
- Rx
- fingers